

[4]

- Q.6 Attempt any two:
- i. Design a combinational logic using PLA which produce 3 different outputs which represent following function. **5**  
 $F1 = \sum (1,4,5,12,14,15)$   
 $F2 = \sum (3,5,6,8,10,13)$   
 $F3 = \sum (0,2,7,11,14,15)$
- ii. Realize the expression **5**  
 $Y1 = AB'C + BC'D' + A'CD'$ ,  
 $Y2 = BC'D + ABCD + A'C'$ ,  
 $Y3 = AD' + BC'D + ACD$  with MUXs, Decoder, Gates and ROM.
- iii. What are the different tools for creating a state machine on Chip? **5**  
Explain all in brief.

\*\*\*\*\*

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrolment No.....



Faculty of Engineering  
End Sem (Odd) Examination Dec-2017  
CS2OE01 Digital Electronics

Programme: Diploma

Branch/Specialisation: CS

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. The output of a logic gate is 1 when all its inputs are at logic 0. the gate is either **1**  
(a) a NAND or an EX-OR (b) an OR or an EX-NOR  
(c) an AND or an EX-OR (d) a NOR or an EX-NOR
- ii. DeMorgan's first theorem shows the equivalence of **1**  
(a) OR gate and Exclusive OR gate.  
(b) NOR gate and Bubbled AND gate.  
(c) NOR gate and NAND gate.  
(d) NAND gate and NOT gate
- iii. In a JK Flip-Flop, toggle means **1**  
(a) Set Q = 1 and Q = 0.  
(b) Set Q = 0 and Q = 1.  
(c) Change the output to the opposite state.  
(d) No change in output.
- iv. Two bit subtraction is done by **1**  
(a) Demultiplexer (b) Multiplexer  
(c) Full subtract (d) Half subtract
- v. How many flip flops are required to construct a decade counter **1**  
(a) 10 (b) 3 (c) 4 (d) 2
- vi. ASM chart takes entire block as **1**  
(a) 1 unit (b) 2 unit (c) 3 unit (d) 4 unit
- vii. Which of the following is the fastest logic **1**  
(a) TTL (b) ECL (c) CMOS (d) LSI

P.T.O.

[2]


- viii. Table that is not a part of asynchronous analysis procedure is 1  
 (a) Transition table (b) State table  
 (c) Flow table (d) Excitation table
- ix. Which of the memory is volatile memory 1  
 (a) ROM (b) RAM (c) PROM (d) EEPROM
- x. The access time of ROM using bipolar transistors is about 1  
 (a) 1 sec (b) 1 msec (c) 1 microsec (d) 1 nsec.

- Q.2 i. Convert The following number in Hexadecimal, Binary and Octal 2  
 (56)<sub>10</sub>
- ii. Minimize the following expression using K-Map & realize it with NAND Gates. 3  
 $F = A'B'C'D + A'BC'D + A'B'CD + ABCD' + ABC'D$
- iii. Design a BCD to Excess-3 Code converter combinational Circuit. 5
- OR iv. Design a combination circuit which can compare two bits long digital number. 5

- Q.3 i. Explain the working of JK flip-flop. What is the Race-Around Condition? 2
- ii. Design a 4-bit bidirectional shift register and explain its clock diagram in detail. 8
- OR iii. What is Synchronous system? Define the meaning of synchronous state machine. What are the steps of analyzing state machine? 8


- Q.4 i. Design a self starting counter that generate following 3 bit sequence 3  
 000, 010, 001, 100, 110, 101, 111, 011
- ii. Assuming that data changes on positive clock transition, construct an AST to implement the state diagram of given figure. Use MUX for IFL & Gate for OFL. 7

[3]

 

- OR iii. Construct a reduced state diagram for a system that checks an input line to find the word 110110. The check begins in synchronism with the start of a word and repeat at 6-bit interval. 7

 - Q.5 i. For a synchronous circuit given in below figure 4




Draw the fundamental mode model and label the feedback variables and excitation variable. Also draw the excitation table for circuit.

- ii. Compare all logic families in tabular form. 6
- OR iii. Explain the interfacing of TTL to CMOS and CMOS to TTL logic. 6

CS2OE01 Digital Electronics  
Marking Scheme


Q.1	i. The output of a logic gate is 1 when all its inputs are at logic 0. the gate is either (d) a NOR or an EX-NOR	1	iii. Design a BCD to Excess-3 Code converter combinational Circuit. <b>BCD to EX-3 Code – 3 marks</b> <b>K-map Solution – 1 mark</b> <b>Convertor Diagram – 1 mark</b>	5
	ii. DeMorgan's first theorem shows the equivalence of (b) NOR gate and Bubbled AND gate.	1	OR iv. Design a combination circuit which can compare two bits long digital number. <b>Comparator Table – 1 mark</b> <b>Comparator Equation – 3 marks</b> <b>Circuit Diagram – 1 mark</b>	5
	iii. In a JK Flip-Flop, toggle means (c) Change the output to the opposite state.	1		
	iv. Two bit subtraction is done by (d) Half subtract	1		
	v. How many flip flops are required to construct a decade counter (c) 4	1	Q.3 i. Explain the working of JK flip-flop. What is the Race-Around Condition? <b>JK flip-flop and Race-Around Condition – 2 marks</b>	2
	vi. ASM chart takes entire block as (a) 1 unit	1	ii. Design a 4-bit bidirectional shift register and explain its clock diagram in detail. <b>Register and its types – 5 marks</b> <b>Bidirectional shift register – 3 marks</b>	8
	vii. Which of the following is the fastest logic (b) ECL	1	OR iii. What is Synchronous system? Define the meaning of synchronous state machine. What are the steps of analyzing state machine? <b>Synchronous system – 2 marks</b> <b>Synchronous state machine – 3 marks</b> <b>Steps of analyzing state machine – 3 marks</b>	8
	viii. Table that is not a part of asynchronous analysis procedure is (d) Excitation table	1		
	ix. Which of the memory is volatile memory (b) RAM	1	Q.4 i. Design a self starting counter that generate following 3 bit sequence 000, 010, 001, 100, 110, 101, 111, 011 <b>Converter table and state diagram – 1 mark</b> <b>K-map for input – 1 mark</b> <b>Black diagram – 1 mark</b>	3
	x. The access time of ROM using bipolar transistors is about (c) 1 microsec	1	ii. Assuming that data changes on positive clock transition, construct an AST to implement the state diagram of given figure. Use MUX for IFL & Gate for OFL.	7
Q.2	i. Convert The following number in Hexadecimal, Binary and Octal (56) <sub>10</sub> <b>Hexadecimal: (38)<sub>16</sub>,</b> <b>Binary: (111000)<sub>2</sub> and</b> <b>Octal: (70)<sub>8</sub></b>	2		
	ii. Minimize the following expression using K-Map & realize it with NAND Gates. $F = A'B'C'D + A'BC'D + A'B'CD + ABCD' + ABC'D$ <b>F = A'B'D + BC'D + ABCD' – 2 marks</b> <b>Realization with NAND – 1 mark</b>	3		

 

Asynchronous state table for given problem – 3 marks  
Use MUX for IFL/OFL – 4 marks

- OR iii. Construct a reduced state diagram for a system that checks an input line to find the word 110110. The check begins in synchronism with the start of a word and repeat at 6-bit interval.  
State diagram – 3 marks  
State table – 2 marks  
System diagram – 2 marks

 - Q.5 i. For a synchronous circuit given in below figure 4



Draw the fundamental mode model and label the feedback variables and excitation variable. Also draw the excitation table for circuit.

Fundamental mode model – 2 marks  
Excitation table for circuit – 2 marks

- ii. Compare all logic families in tabular form. 6  
Compare logic families – 3 marks  
Table at least five parameters – 3 marks
- OR iii. Explain the interfacing of TTL to CMOS and CMOS to TTL logic. 6  
Interfacing – 2 marks  
TTL to CMOS – 2 marks  
CMOS to TTL – 2 marks
- Q.6 Attempt any two:
- i. Design a combinational logic using PLA which produce 3 different outputs which represent following function. 5  
 $F1 = \sum (1,4,5,12,14,15)$   
 $F2 = \sum (3,5,6,8,10,13)$   
 $F3 = \sum (0,2,7,11,14,15)$   
PLA with F1, F2 and F3 – 5 marks
- ii. Realize the expression 5  
 $Y1 = AB'C + BC'D' + A'CD'$ ,  
 $Y2 = BC'D + ABCD + A'C'$ ,  
 $Y3 = AD' + BC'D + ACD$  with MUXs, Decoder, Gates and ROM.  
Realize expression Y1, Y2 and Y3 – 1 mark  
MUX – 1 mark  
Decoder – 1 mark  
Gates – 1 mark  
ROM – 1 mark
- iii. What are the different tools for creating a state machine on Chip? 5  
Explain all in brief.  
Tools for creating a state machine – 3 marks  
VHDL, Verilog – 2 marks

\*\*\*\*\*