

[4]

- Q.6 i. Explain the working of CMOS inverter with proper diagram. 3
ii. Explain the working of TTL Tristate logic with neat and clean diagram. 7
OR iii. What are the constraints in interfacing TTL with CMOS and vice-versa? Explain with suitable diagrams. 7

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2017
CS3ES10 / EC3CO07 / EI3CO07 / IT3ES10
Digital Electronics / Digital Circuit & Systems

Programme: B.Tech.

Branch/Specialisation: CS/EC/EI/IT

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. Which is the decimal equivalent of largest possible 16 bit binary number? 1
(a) 65536 (b) 65535 (c) 32768 (d) 32767
ii. What should be the Boolean expression for L in Figure 1? 1

 


Figure 1

- (a) $(W \cdot X) + Y + \bar{Z}$ (b) $(W \cdot X) + \bar{Y} \cdot Z$
(c) $(W + X) + (\bar{Y} \cdot Z)$ (d) $(W + X) \cdot Y \cdot \bar{Z}$
- iii. Economically how many 2-input NAND gates are required to implement the Boolean function $Y = \bar{A} \cdot B + C$? 1
(a) 2 (b) 3 (c) 4 (d) 5
- iv. How many inputs a decimal to BCD Encoder should have? 1
(a) 4 (b) 10 (c) 8 (d) 16
- v. In a J-K flip flop the condition $K = \bar{J}$ is used to implement. 1
(a) D flip flop (b) S-R flip flop
(c) T flip flop (d) Master-slave flip flop

P.T.O.

[2]

- vi. Statement 1: Mealy machine reacts faster to inputs. Statement 2: Moore machine has more circuit delays. Choose the correct option: **1**
 (a) Both statements are true
 (b) Statement 1 is true but Statement 2 is false
 (c) Statement 1 is false and Statement 2 is true
 (d) Both statements are false
- vii. A Programmable Logic Array consists of **1**
 (a) Programmable AND array and fixed OR array
 (b) Fixed AND array and programmable OR array
 (c) Programmable AND array and programmable OR array
 (d) None of these.
- viii. If a RAM chip has 12 address input lines then it can access memory locations up to. **1**
 (a) 1k (b) 2k (c) 3k (d) 4k
- ix. To drive capacitive loads a TTL circuit is modified to have. **1**
 (a) Active pull-down element (b) Active pull-up element
 (c) Both the elements (d) None of these
- x. Which of the following logic family has least power consumption? **1**
 (a) DTL (b) TTL (c) RTL (d) CMOS

Q.2 i. A logic circuit implements the following Boolean function. **3**

$$f(w, x, y, z) = \bar{w}y + w\bar{y}\bar{z}$$

It is found that the circuit input combination $w = y = 1$ can never occur. Find a simpler expression for f using proper don't care conditions.

ii. Use K-map to expand the following switching function to canonical SOP form. **7**

$$F(A, B, C) = (\bar{A} + B)(A + B + \bar{C})(\bar{A} + C)$$

OR iii. Use Quine-McCluskey method to minimize the following function. **7**

$$f(w, x, y, z) = \sum m(1,4,7,10,13) + d(5,14,15)$$

[3]

- Q.3 i. Differentiate between Multiplexer and Demultiplexer. **2**
 ii. For the timing diagram shown in Figure 2, find both a minimum NAND and a minimum NOR realization of function $f(A, B, C)$. Use DeMorgan's theorem to show proper Boolean expressions **8**

 


Figure 2

utilized to make such realization.

OR iii. Explain and design a BCD to Excess-3 code converter with its block diagram, truth table, expressions and logic diagram. **8**

Q.4 Attempt any two:

- i. How S-R flip flop can be converted into J-K flip flop? Explain with the help of excitation table, expressions and logic diagram. **5**
 ii. Design a MOD-3 synchronous up counter with the help of state diagram, excitation table, Boolean expressions and logic circuit. **5**
 iii. With the help of state diagram, present-next state table expressions and logic diagram design a sequence detector circuit that produces an output '1' whenever an overlapping sequence 101 occurs. **5**

Q.5 i. Differentiate between SRAM and DRAM. **4**

ii. Explain Read Only Memory. Implement the 3-input functions $f_0 = \sum m(0,2,5,7)$, $f_1 = \sum m(1,3,4,6)$ and $f_2 = \sum m(3,4,5)$ using a ROM. **6**

OR iii. Explain PAL with a suitable example. What is its drawback over PLA? **6**

CS3ES10 / EC3CO07 / EI3CO07 / IT3ES10
Digital Electronics / Digital Circuit & Systems

Marking Scheme

Q.1	i. Which is the decimal equivalent of largest possible 16 bit binary number? (b) 65535	1	OR	iii. Table – 1 (No. of 1's) – 1 mark Table – 2 (2 cell combination) – 2 marks Table – 3 (4 cell combination) – 2 marks Table 4 (essential prime implicant) – 1 mark Final exp. – 1 mark	7	
	ii. What should be the Boolean expression for L in Figure 1? (d) $(W + X) \cdot Y \cdot \bar{Z}$	1				
	iii. Economically how many 2-input NAND gates are required to implement the Boolean function $Y = \bar{A} \cdot B + C$? (c) 4	1				
	iv. How many inputs a decimal to BCD Encoder should have? (b) 10	1				
	v. In a J-K flip flop the condition $K = \bar{J}$ is used to implement. (a) D flip flop	1				
	vi. Statement 1: Mealy machine reacts faster to inputs. Statement 2: Moore machine has more circuit delays. Choose the correct option: (a) Both statements are true	1				
	vii. A Programmable Logic Array consists of (c) Programmable AND array and programmable OR array	1				
	viii. If a RAM chip has 12 address input lines then it can access memory locations up to. (d) 4k	1				
	ix. To drive capacitive loads a TTL circuit is modified to have. (b) Active pull-up element	1				
	x. Which of the following logic family has least power consumption? (d) CMOS	1				
Q.2	i. For proper don't care form definition – 2 marks For final expression – 1 mark	3				
	ii. For correct K-map – 3 marks For proper canonical form (SOP) – 4 marks	7				
				Q.3	i. Each proper difference has 1 mark (1 mark * 2 = 2 marks) ii. Expression of f - 2 marks For each realization- 3 marks. (3 marks * 2 = 6 marks)	2 8
				OR	iii. Block diagram, truth table, expressions and logic diagram - 2 marks each (2 marks * 4 = 8 marks)	8
				Q.4	i. Excitation table- 2 marks Expressions- 2 marks Logic diagram- 1 mark. ii. State diagram- 1 mark State table- 2 marks Expression-1 mark Logic diagram- 1 mark iii. State diagram- 2 marks State table- 1 mark Expression-1 mark Logic diagram-1 mark.	5 5 5
				Q.5	i. Each Proper difference has 1 mark (1 mark * 4 = 4 marks) ii. Definition- 3 marks Function implementation- 1 mark each (1 mark * 3 = 3 marks)	4 6 6
				OR	iii. Explanation of PAL- 2 marks Example- 2 marks Drawbacks- 2 marks	6
				Q.6	i. Diagram- 1 mark Working- 2 marks. ii. Diagram- 3 marks Working- 4 marks. iii. Each interfacing has – 3.5 marks with proper diagram & constraints specified (3.5 marks * 2 = 7 marks)	3 7 7