

[4]

- Q.6 i. Draw the block diagram of feedback scheme. Why negative feedback is more advantageous than positive feedback. **4**
- ii. Explain various feedback topologies? Give expressions for input & output resistances. **6**
- OR iii. What is the criterion for oscillation? Explain the working of wein bridge oscillator & deduce the expression for oscillator frequency. **6**

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2017
EC3CO03 / EI3CO03 Electronic Devices and Circuits
Programme: B.Tech. Branch/Specialisation: EC/EI
Duration: 3 Hrs. **Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. At very high temperature the extrinsic semiconductor become intrinsic because **1**
- (a) Drive in diffusion of dopants & carrier
(b) Band to band transition dominants over impurity ionization
(c) Impurity ionization dominants over band to band transition
(d) Band to band transition is balanced by impurity ionization
- ii. In a Zener diode **1**
- (a) The forward current is very high
(b) Sharp breakdown occurs at a certain reverse voltage
(c) The ratio of V-I can be negative
(d) There are two p-n junctions
- iii. In a bipolar transistor which current is largest **1**
- (a) I_C (b) I_E (c) I_B (d) None of these
- iv. The most commonly used transistor configuration is **1**
- (a) Common emitter (b) Common base
(c) Common collector (d) None of these
- v. A JFET is a _____ driven device. **1**
- (a) Voltage (b) Current
(c) Both (a) & (b) (d) None of these
- vi. A MOSFET differs from a JFET mainly because **1**
- (a) Of power rating (b) The MOSFET has two stages
(c) The JFET has p-n junction (d) None of the above

P.T.O.


[2]

- vii. The main features of a large signal amplifier circuit is **1**
 (a) Power efficiency
 (b) Max power limitation
 (c) Impedance matching to the output devices
 (d) All of these
- viii. A two transistor class B power amplifier is commonly called _____ amplifier. **1**
 (a) Dual (b) Push-pull
 (c) Symmetrical (d) Differential
- ix. The value of negative feedback fraction is always **1**
 (a) Less than 1 (b) More than 1
 (c) Equal to one (d) One
- x. An oscillator employs _____ feedback **1**
 (a) Positive
 (b) Negative
 (c) Neither negative nor positive
 (d) None of these

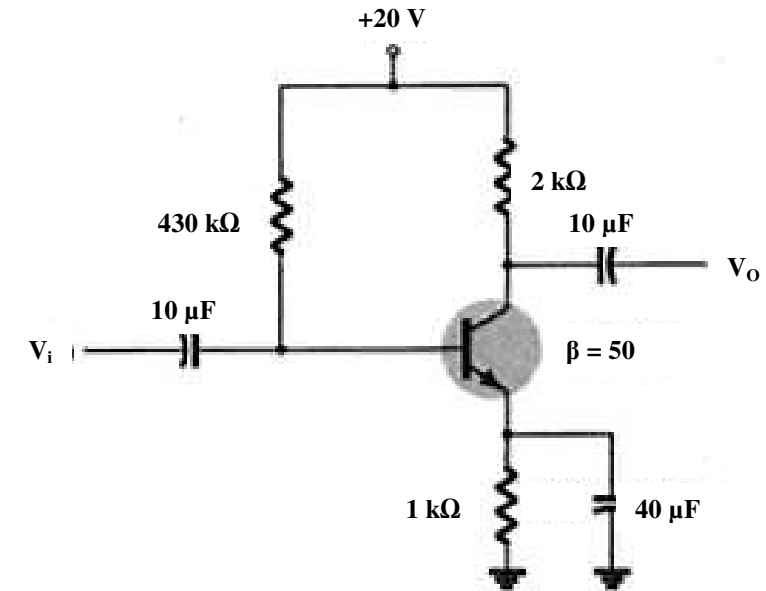- Q.2 i. What is Hall effect? **2**
 ii. Explain V-I characteristics of Zener diode with both types of breakdowns. **3**
 iii. Explain PN junction diode with respect to following points- **5**
 (a) Application (b) Effect of temperature-change
- OR iv. Explain working of any one full wave rectifier. Give expressions for: **5**
 (a) Rectifier efficiency (b) Ripple factor
- Q.3 i. Give relation between α , β & γ of BJT. **2**
 ii. Why is biasing required in BJT? Which biasing circuit is mostly used & why? **3**
 iii. Explain the H-parameter model of transistor & Derive the expression of current gain & voltage gain. **5**

[3]

- OR iv For the silicon transistor Find the value of **5**
 $I_C, I_B, I_E, V_B, V_C, V_E, V_{CE}, V_{BC}$. The figure is shown below.



- Q.4 i. Explain construction & working of N-channel JFET. When is pinch off condition reached? **4**
 ii. Draw and explain the drain & transfer characteristics of JFET with different regions of operations. **6**
- OR iii. Draw a neat labelled schematic diagram of depletion type MOSFET & Explain its working. **6**
- Q.5 i. Why bootstrapping is required in a BJT based amplifier circuit? Explain with neat labelled diagram. **4**
 ii. Describe the working of a class-B amplifier & calculate its power & efficiency. **6**
- OR iii. What are push pull amplifier? A class B push pull power amplifier is supplied with $V_{CC} = 50V$. The signal swings the collector voltage down $V_{min} = 5V$. The total power dissipation in both transistors is 40 W. Find the total power & conversion efficiency. **6**

P.T.O.

EC3CO03 / EI3CO03 Electronic Devices and Circuits

Marking Scheme

Q.1	i.	(b) Band to band transition dominants over impurity ionization	1
	ii.	(b) Sharp breakdown occurs at a certain reverse voltage	1
	iii.	(b) I_E	1
	iv.	(a) Common emitter	1
	v.	(a) Voltage	1
	vi.	(c) The JFET has p-n junction	1
	vii.	(d) All of these	1
	viii.	(b) Push-pull	1
	ix.	(a) Less than 1	1
	x.	(a) Positive	1
Q.2	i.	1 mark for diagram 1 mark for explanation	2
	ii.	1 mark for V-I characteristics diagram 2 marks for breakdowns.	3
	iii.	2.5 marks for Application 2.5 marks for effect of temperature-change	5
OR	iv.	2 marks for working 1 mark for rectifier efficiency 1 marks for ripple factor 1 mark for diagram	5
Q.3	i.	2 marks for relation between α , β & γ of BJT.	2
	ii.	1 marks for reason for biasing 2 marks for type mostly used.	3
	iii.	2 marks for H-parameter model diagram & equation, 1.5 marks for current gain 1.5 marks for voltage gain	5
OR	iv	2 marks for I_C, I_B, I_E , 2 marks for V_B, V_C, V_E , 1 mark for V_{CE}, V_{BC}	5
		Ans- $I_B = 40.1 \mu A$ $I_C = 2.01 \text{ mA}$ $I_E = 2.05 \text{ mA}$ $V_B = 2.71 \text{ V}$ $V_C = 15.98 \text{ V}$ $V_E = 2.01 \text{ V}$ $V_{CE} = 13.97 \text{ V}$ $V_{BC} = -13.27 \text{ V}$	

Q.4	i.	1 mark for construction 2 marks for working of N-channel JFET 1 mark for condition asked	4
	ii.	2 marks for drain characteristics of JFET 1 mark for transfer characteristics of JFET 3 marks for region explanation	6
OR	iii.	2 marks for diagram of depletion type MOSFET 4 marks for its working	6
Q.5	i.	1.5 marks for diagram 2.5 marks for explanation.	4
	ii.	2 marks for working 2 marks for power calculation 2 marks for efficiency calculation.	6
OR	iii.	2 marks for push pull amplifier 2 marks for total power 2 marks for efficiency $P_{in}(dc)=136.45 \text{ W}$ $P_{out}(ac)=99.65 \text{ W}$ $\eta=73.03\%$	6
Q.6	i.	1 marks for diagram 3 marks for advantages.	4
	ii.	3 marks for various topologies 3 marks for expression.	6
OR	iii.	1 mark for criterion 3 marks for wein bridge 2 marks for oscillator frequency.	6