

[4]

- OR iii. Describe the current commutated chopper with waveforms and equivalent circuits. Write the applications of voltage commutated chopper. **6**
- Q.6 i. Draw the single phase bidirectional ac voltage controller with RL load and explain its working principle with waveforms. **4**
- ii. A single phase half wave ac voltage controller is connected with a load of  $R = 20\Omega$  with an input voltage of 230V, 50Hz. If the firing angle of thyristor is  $90^\circ$ . Determine: **6**
- (a) RMS output voltage  
(b) Power delivered to load,  
(c) Average value of thyristor current  
(d) Average value of diode current
- OR iii. Discuss the operating principle of single phase to single phase step-down cycloconverter using midpoint converters. Mention the conduction of various thyristors in the waveforms. **6**

\*\*\*\*\*

Total No. of Questions: 6

Total No. of Printed Pages:4



Enrollment No.....

Faculty of Engineering

End Sem (Even) Examination May-2018

EE3CO02/ EX3CO02 Power Electronics Devices & Circuits

Programme: B.Tech.

Branch/Specialisation: EE/EX

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. Turn on time of an SCR can be decreased by using a **1**
- (a) Rectangular pulse of high amplitude and narrow width  
(b) Triangular pulse  
(c) Rectangular pulse of low amplitude and wide width  
(d) Trapezoidal pulse
- ii. In dynamic equalising circuit for series connected thyristors, the value of C is depends on **1**
- (a) Reverse recovery characteristics  
(b) Turn off characteristics  
(c) Turn on characteristics  
(d) Rise time characteristics
- iii. In a single phase full bridge converter, the average dc output voltage is equal to **1**
- (a)  $V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2V} \sin \omega t . d\omega t$   
(b)  $V_o = \frac{1}{\pi} \int_0^{\pi+\alpha} \sqrt{2V} \sin \omega t . d\omega t$   
(c)  $V_o = \frac{1}{\pi} \int_{\alpha}^{2\pi+\alpha} \sqrt{2V} \sin \omega t . d\omega t$   
(d)  $V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2V} \sin \omega t . d\omega t$
- iv. The firing angle  $\alpha$ , the dc output voltage of three phase full bridge converter is, **1**
- (a)  $\frac{3\sqrt{3}V_m}{\pi} \cos \alpha$  (b)  $\frac{\sqrt{3}V_m}{2\pi} \cos \alpha$   
(c)  $\frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$  (d)  $\frac{3V_m}{\pi} \cos \alpha$

P.T.O.

[2]

- v. A single phase full bridge voltage source inverter operates with R load, nature of output current is ..... **1**  
 (a) Square wave (b) Sinewave (c) Triangular wave (d) Pulse wave
- vi. In MC murray commutation inverter circuit, the circuit turnoff time is **1**  
 (a) Independent of load current and depend on operating frequency  
 (b) Depend on load current and independent on operating frequency  
 (c) Depend on load current and also load power factor  
 (d) Independent of load current and depend on recovery period
- vii. The output voltage of dc to dc converter can be controlled by **1**  
 (a) Amplitude modulation  
 (b) Frequency modulation  
 (c) Pulse width modulation  
 (d) Pulse width and frequency modulation
- viii. In step up chopper, input voltage is 200V and output voltage is 400V. If the conduction time of semiconductor switch is 150 μs, the non-conducting time of semiconductor switch is..... **1**  
 (a) 150μs (b) 200μs (c) 250μs (d) 300μs
- ix. Average value of output voltage of half wave ac voltage controller at firing angle α is equal to **1**  
 (a) 0 (b)  $\frac{\sqrt{2}V}{2\pi}(\cos \alpha - 1)$   
 (c)  $\frac{\sqrt{2}V}{2\pi}(\cos \alpha + 1)$  (d)  $\frac{\sqrt{2}V}{\pi}(\cos \alpha - 1)$
- x. A three phase to three phase cycloconverter using three phase bridge converter requires **1**  
 (a) 18 SCRs (b) 36 SCRs (c) 6 SCRs (d) 12 SCRs
- Q.2 i. Write a short note on **3**  
 (a) Over Voltage protection (b) Over current protection  
 (c) Gate protection
- ii. What are the different triggering circuits of a SCR? Draw a resistance triggering circuit and explain its operation. What is the limitation of a R triggering circuit. **7**

[3]

- OR iii. Draw the V-I characteristics of a TRIAC and explain different operating regions. What are the applications of TRIAC? **7**
- Q.3 i. A single phase fully controlled bridge converter is supplied from 220V, 50 Hz ac supply and fed to a load which consists of R=12 ohm and large inductance so that load current is constant. If the firing angle is 45°, calculate (a) average output voltage, (b) average output current, (c) average current of thyristor, (d) RMS current of thyristor **4**
- ii. With a neat circuit diagram describe the circulating and non-circulating mode of a dual converter. Draw the voltage waveforms of dual converter. **6**
- OR iii. Draw the circuit diagram and waveform of three phase bridge converter with RL load. Explain its working principle at α=30°. **6**
- Q.4 i. Define inverter. What are the types of inverter? What are the applications of inverter circuit? **3**
- ii. Draw the circuit diagram of a single phase half bridge voltage source inverter with RL load and explain its operating principle and derive the expression for (a) RMS value of output voltage (b) RMS output load current. **7**
- OR iii. Discuss the operating principle of a three phase bridge inverter with a suitable diagram and waveform when each thyristor conducts for 180°. **7**
- Q.5 i. Input to the step up chopper is 200 V. The output required is 600 V. If the conducting time of thyristor is 200 μsec. Compute (a) Chopping frequency, (b) If the pulse width is halved for constant frequency of operation, find the new output voltage. **4**
- ii. Draw the circuit diagram of step up down chopper and describe its operating principle. Draw the voltage and current waveforms of step up and down chopper. Derive expressions for average output voltage and rms output voltage. What are the applications of step up and down chopper? **6**

P.T.O.

## Marking Scheme

### EE3CO02/ EX3CO02 Power Electronics Devices & Circuits

Q.1	i. Turn on time of an SCR can be decreased by using a (a) Rectangular pulse of high amplitude and narrow width	<b>1</b>			
	ii. In dynamic equalising circuit for series connected thyristors, the value of C is depends on (a) Reverse recovery characteristics	<b>1</b>			
	iii. In a single phase full bridge converter, the average dc output voltage is equal to (d) $V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2V} \sin \omega t . d\omega t$	<b>1</b>			
	iv. The firing angle $\alpha$ , the dc output voltage of three phase full bridge converter is, (a) $\frac{3\sqrt{3}V_m}{\pi} \cos \alpha$	<b>1</b>			
	v. A single phase full bridge voltage source inverter operates with R load, nature of output current is ..... (a) Square wave	<b>1</b>			
	vi. In MC murray commutation inverter circuit, the circuit turnoff time is (b) Depend on load current and independent on operating frequency	<b>1</b>			
	vii. The output voltage of dc to dc converter can be controlled by (d) pulse width and frequency modulation	<b>1</b>			
	viii. In step up chopper, input voltage is 200V and output voltage is 400V. If the conduction time of semiconductor switch is 150 $\mu$ s, the non-conducting time of semiconductor switch is..... (a) 150 $\mu$ s	<b>1</b>			
	ix. Average value of output voltage of half wave ac voltage controller at firing angle $\alpha$ is equal to (b) $\frac{\sqrt{2V}}{2\pi} (\cos \alpha - 1)$	<b>1</b>			
	x. A three phase to three phase cycloconverter using three phase bridge converter requires (b) 36 SCRs	<b>1</b>			
Q.2	i. Write a short note on (a) Over Voltage protection (b) Over current protection (c) Gate protection	1 mark 1 mark 1 mark	<b>3</b>		
	ii. Different triggering circuits of a SCR Circuit diagram Waveform Limitation of an R triggering circuit.	2 marks 2 marks 2 marks 1 mark	<b>7</b>		
OR	iii. V-I characteristics of a TRIAC Different operating regions. Applications of TRIAC.	2 marks 3 marks 2 marks	<b>7</b>		
Q.3	i. (a) Average output voltage=140.1V (b) Average output current= 11.65A (c) Average current of thyristor= 5.8375A (d) RMS current of thyristor= 8.256A	1 mark 1 mark 1 mark 1 mark	<b>4</b>		
	ii. Circuit diagram of the circulating and non-circulating mode of a dual converter. Draw the voltage waveforms of dual converter.	3 marks 3 marks	<b>6</b>		
OR	iii. Circuit diagram Waveform. Working principle	2 marks 2 marks 2 marks	<b>6</b>		
Q.4	i. Define inverter. Types of inverter Application of inverter circuit	1 mark 1 mark 1 mark	<b>3</b>		
	ii. Circuit diagram Waveform (i) RMS value of output voltage (ii) RMS output load current.	1 mark 2 marks 2 marks 2 marks	<b>7</b>		
OR	iii. circuit diagram Waveform Explanation with derivation	2 marks 3 marks 2 marks	<b>7</b>		
Q.5	i. Chopping frequency=3.33kHz If the pulse width is halved for constant frequency of operation, find the new output voltage=300V	2 marks 2 marks	<b>4</b>		

	ii.	Circuit diagram	1 mark	<b>6</b>
		Voltage and current waveforms	2 marks	
		Expressions for average output voltage and rms output voltage.	2 marks	
		Applications of step up and down chopper	1 mark	
OR	iii.	Circuit Diagram of current commutated chopper	2 marks	<b>6</b>
		Waveforms and equivalent circuits	2 marks	
		Applications of voltage commutated chopper.	2 marks	
Q.6	i.	Circuit diagram	2 marks	<b>4</b>
		Voltage and current waveforms	2 marks	
	ii.	(a) RMS output voltage = 199.185V	1.5 marks	<b>6</b>
		(b) power delivered to load= 1983.73watt	1.5 marks	
		(c) average value of thyristor current = 2.587A	1.5 marks	
		(d) average value of diode current= -5.174A	1.5 marks	
OR	iii.	Circuit diagram	2 marks	<b>6</b>
		Voltage and current waveforms	2 marks	
		Explanation	2 marks	

\*\*\*\*\*