

Total No. of Questions: 6

Total No. of Printed Pages:3

Enrollment No.....



Faculty of Engineering  
End Sem (Odd) Examination Dec-2018  
EE3CO23/EX3CO23 Analog Electronics

Programme: B.Tech.

Branch/Specialisation: EE/EX

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1
- i. To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to which junction? **1**  
(a) Collector-emitter (b) Base-collector  
(c) Base-emitter (d) Collector-base
  - ii. A JFET is a ..... driven device **1**  
(a) Current (b) Voltage  
(c) Both (a) and (b) (d) None of these
  - iii. Which of the following is referred to as the reverse transfer voltage ratio? **1**  
(a)  $h_i$  (b)  $h_r$  (c)  $h_f$  (d)  $h_o$
  - iv. A common-emitter amplifier has \_\_\_\_\_ voltage gain, \_\_\_\_\_ current gain, \_\_\_\_\_ power gain, and \_\_\_\_\_ input impedance. **1**  
(a) High, low, high, low (b) High, high, high, low  
(c) High, high, high, high (d) Low, low, low, high
  - v. When a differential amplifier is operated single-ended, \_\_\_\_\_ **1**  
(a) The output is grounded  
(b) One input is grounded and signal is applied to the other  
(c) Both inputs are connected together  
(d) The output is not inverted
  - vi. A voltage follower ..... **1**  
(a) Has a voltage gain of 1 (b) Is non-inverting  
(c) Has no feedback resistor (d) Has all of these

P.T.O.

[2]

- vii. Find the output voltage of the log-amplifier **1**  
 (a)  $V_O = -(kT/q) \times \ln(V_i/V_{ref})$  (b)  $V_O = -(kT/q) \times \ln(V_i/V_{ref})$   
 (c)  $V_O = -(kT/q) \times \ln(V_{ref}/V_i)$  (d)  $V_O = (kT/q) \times \ln(V_i/V_{ref})$
- viii. Zero crossing detectors is also called as **1**  
 (a) Square to sine wave generator  
 (b) Sine to square wave generator  
 (c) Sine to triangular wave generator  
 (d) All of these
- ix. Pin 8 of 555 timer IC consist of **1**  
 (a) Voltage supply (b) Output  
 (c) Ground (d) Discharge
- x. In an unregulated power supply, if load current increases, the output voltage ..... **1**  
 (a) Remains the same (b) Decreases  
 (c) Increases (d) None of these
- Q.2 i. Define stability factor with reference to transistor biasing. State the factors affecting the stability. **2**  
 ii. In a certain transistor, collector current is 0.98mA and base current is 20mA. Determine the values of **3**  
 (a) Emitter current (b) Current amplification factor ( $\beta$ )  
 (c) Current gain factor
- iii. Explain enhancement type MOSFET under to following heads: **5**  
 (a) Construction  
 (b) Operation  
 (c) Characteristics (Drain and transfer)
- OR iv. Why CE configuration is most popular in amplifier circuits? Draw its circuit diagram. Explain the output characteristics with indication of the active, saturation and cut off region. **5**
- Q.3 Attempt any two:  
 i. Why negative feedback is preferred over positive feedback. Draw different feedback topology with their input and output expression. **5**

[3]

- ii. With the help of circuit diagram, explain the working of class B push-pull amplifier. Also, mention its advantages and applications. **5**
- iii. Draw circuit diagram and explain working principle of **5**  
 (a) Colpitt's Oscillator (b) Hartley Oscillator
- Q.4 i. The op-amp is used in the inverting and non-inverting mode with  $R_1 = 2K\Omega$  and  $R_F = 100K\Omega$ . If  $V_{cc} = \pm 15V$  and rms input value  $V_i = 20mv$ , calculate the output voltage in each case. **2**  
 ii. What is an op-amp? Write the characteristics of an ideal op-amp. **3**  
 iii. Define following parameters **5**  
 (a) CMRR (b) PSRR (c) Slew rate  
 (d) Input offset current (e) Output offset voltage
- OR iv. Derive expression of closed loop voltage gain for inverting and non-inverting amplifier. **5**
- Q.5 i. Derive output expression (closed loop configuration) for summing amplifier. **2**  
 ii. Draw and explain second order high pass butterworth filter with frequency response. **3**  
 iii. Draw integrator and differentiator circuit. Derive their output voltage expression with suitable output waveform. **5**
- OR iv. What is the main difference between square wave generator and Schmitt trigger? Explain Schmitt trigger with suitable waveform. Write its effects of hysteresis. **5**
- Q.6 i. Compare LM78XX and LM317 regulators. **2**  
 ii. Draw and explain block diagram of three pin IC voltage regulator. **3**  
 iii. What is the necessity of SMPS? Draw and explain the block diagram of SMPS. Write its applications. **5**
- OR iv. Draw the circuit of astable multivibrator using 555 timer. Explain its operation and sketch the relevant waveform. **5**

\*\*\*\*\*

**Marking Scheme**  
**EE3CO23/EX3CO23 Analog Electronics**

Q.1	i.	To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to which junction? (d) Collector-base	<b>1</b>
	ii.	A JFET is a ..... driven device (b) Voltage	<b>1</b>
	iii.	Which of the following is referred to as the reverse transfer voltage ratio? (b) $h_r$	<b>1</b>
	iv.	A common-emitter amplifier has _____ voltage gain, _____ current gain, _____ power gain, and _____ input impedance. (b) High, high, high, low	<b>1</b>
	v.	When a differential amplifier is operated single-ended, _____ (b) One input is grounded and signal is applied to the other	<b>1</b>
	vi.	A voltage follower ..... (d) Has all of these	<b>1</b>
	vii.	Find the output voltage of the log-amplifier (b) $V_O = -(kT/q) \times \ln(V_i/V_{ref})$	<b>1</b>
	viii.	Zero crossing detectors is also called as (b) Sine to square wave generator	<b>1</b>
	ix.	Pin 8 of 555 timer IC consist of (a) Voltage supply	<b>1</b>
	x.	In an unregulated power supply, if load current increases, the output voltage ..... (b) Decreases	<b>1</b>
Q.2	i.	Stability factor <span style="float: right;">1 mark</span> Factors affecting the stability (at least 2) <span style="float: right;">1 mark</span>	<b>2</b>
	ii.	(a) Emitter current <span style="float: right;">1 mark</span> (b) Current amplification factor ( $\beta$ ) <span style="float: right;">1 mark</span> (c) Current gain factor <span style="float: right;">1 mark</span>	<b>3</b>
	iii.	Explain enhancement type MOSFET under to following heads: (a) Construction <span style="float: right;">1 mark</span> (b) Operation <span style="float: right;">2 marks</span> (c) Characteristics (Drain and transfer) <span style="float: right;">2 marks</span>	<b>5</b>

OR	iv.	CE configuration is most popular in amplifier circuits  Circuit diagram. Explanation the output characteristics Indication of the active, saturation and cut off region	<b>5</b>  1 mark 1 mark 2.5 marks 0.5 mark
Q.3	i.	Attempt any two: Preferred Negative feedback to positive feedback Different topology with their input and output expression 1 mark for each (1 mark *4)	<b>5</b> 1 mark 4 marks
	ii.	Construction Circuit diagram Working Advantages Applications	<b>5</b> 1 mark 1 mark 2 marks 0.5 mark 0.5 mark
	iii.	(a) Colpitt's Oscillator Circuit diagram Working principle (b) Hartley Oscillator Circuit diagram Working principle	<b>5</b> 1 mark 1.5 marks 1 mark 1.5 marks
Q.4	i.	Calculate the output voltage in each case. 1 mark for each case	<b>2</b> (1 mark *2)
	ii.	Definition of an op-amp Characteristics of an ideal op-amp	<b>3</b> 1 mark 2 marks
	iii.	Define following parameters 1 mark for each parameters (a) CMRR <span style="float: right;">(b) PSRR</span> (d) Input offset current <span style="float: right;">(c) Slew rate</span> (e) Output offset voltage	<b>5</b> (1 mark *5)
OR	iv	Expression of closed loop voltage gain for inverting  Expression of closed loop voltage gain for non-inverting	<b>5</b> 2.5 marks 2.5 marks
Q.5	i.	Expression (closed loop configuration) for summing amplifier.	<b>2</b>

	ii.	Diagram	0.5 mark	<b>3</b>
		Explanation	2 marks	
		Frequency response	0.5 mark	
	iii.	Draw integrator and differentiator circuit. Derive their output voltage expression with suitable output waveform.		<b>5</b>
		2.5 marks for each	(2.5 mark *2)	
OR	iv	Difference b/w square wave generator and Schmitt trigger		<b>5</b>
			1 mark	
		Explanation	2 marks	
		waveform	1 mark	
		effects of hysteresis	1 mark	
Q.6	i.	Compare LM78XX and LM317 regulators.		<b>2</b>
		At least any two points	(1 mark *2)	
	ii.	Diagram	1 mark	<b>3</b>
		Explanation	2 marks	
	iii.	Necessity of SMPS	1 mark	<b>5</b>
		Draw	1 mark	
		Explanation	2 marks	
		Applications	1 mark	
OR	iv.	Draw the circuit	1 mark	<b>5</b>
		Explanation of its operation	3 marks	
		Waveform	1 mark	

\*\*\*\*\*