

Enrollment No.....



Faculty of Engineering  
End Sem (Odd) Examination Dec-2017  
EE3CO09 / EX3CO09 Electronic Devices and Digital  
Circuits

Programme: B.Tech.

Branch/Specialisation: EE/EX

**Duration: 3 Hrs.****Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.


- Q.1 i.  $I_C = \beta I_B + \dots\dots\dots$  1  
 (a)  $I_{CBO}$  (b)  $I_C$  (c)  $I_{CEO}$  (d)  $\alpha I_E$
- ii. If the value of  $\alpha$  is 0.9, then value of  $\beta$  is  $\dots\dots\dots$  1  
 (a) 9 (b) 0.9 (c) 900 (d) 90
- iii. In an unregulated power supply, if input a.c. voltage increases, the output voltage  $\dots\dots\dots$  1  
 (a) Increases (b) Decreases  
 (c) Remains the same (d) None of these
- iv. A Zener diode is used as a voltage regulating device 1  
 (a) Shunt (b) Series (c) Series-shunt (d) None of these
- v. One condition for oscillation is  $\dots\dots\dots$  1  
 (a) A phase shift around the feedback loop of  $180^\circ$   
 (b) A gain around the feedback loop of one-third  
 (c) A phase shift around the feedback loop of  $0^\circ$   
 (d) A gain around the feedback loop of less than 1
- vi. In Colpitt's oscillator, feedback is obtained  $\dots\dots\dots$  1  
 (a) By magnetic induction  
 (b) By a tickler coil  
 (c) From the centre of split capacitors  
 (d) None of these
- vii. How is a J-K flip-flop made to toggle? 1  
 (a)  $J = 0, K = 0$  (b)  $J = 1, K = 0$   
 (c)  $J = 0, K = 1$  (d)  $J = 1, K = 1$

P.T.O.

[2]

- viii. How many flip-flops are required to make a MOD-32 binary counter? **1**  
 (a) 3 (b) 4 (c) 32 (d) 5
- ix. A 4-bit R/2R digital-to-analog (DAC) converter has a reference of 5 volts. What is the analog output for the input code 0101? **1**  
 (a) 0.3125 V (b) 3.125 V (c) 0.78125 V (d) -3.125 V
- x. What is the major advantage of the R/2R ladder digital-to-analog (DAC), as compared to a binary-weighted digital-to-analog DAC converter? **1**  
 (a) It only uses two different resistor values.  
 (b) It has fewer parts for the same number of inputs.  
 (c) Its operation is much easier to analyze.  
 (d) The virtual ground is eliminated and the circuit is therefore easier to understand and troubleshoot

 - Q.2 i. Draw and explain the Ebers Moll model for PNP transistor. **4**  
 ii. Find the  $I_B$  and  $V_{CE}$  for given circuit. ( $\beta=200$ ,  $V_{BE}=0.7V$ ). **6**



- OR iii. Draw the common emitter amplifier circuit h model and calculate the input impedance, voltage gain in terms of h parameters. **6**

- Q.3 i. Write down the name types of IC regulators. **2**  
 ii. Draw the op-amp based current limiting circuit and explain its working. **3**  
 iii. Draw the SMPS regulator circuit diagram and explain their working with various functional block diagrams. **5**

[3]

- OR iv. Draw the transistor based voltage series and voltage shunt regulators circuit diagram and explain its working. **5**
- Q.4 i. What is Barkhausen Criteria for oscillators? **2**  
 ii. Draw the circuit diagram of phase shift oscillator and explain its Working principal. **3**  
 iii. Draw the circuit diagram of active high pass filter and explain its working principal, also derive the gain expression for it. **5**
- OR iv. Draw the block diagram of 555 timer and explain its working principal. **5**
- Q.5 i. What is race around condition explain and how it remove? **3**  
 ii. Draw the 4 bit ring counter using D flip flop and explain its working. **7**
- OR iv. Design mod 10 decade counter using D flip flop. **7**
- Q.6 i. Write down any 3 difference between analog and digital systems **2**  
 ii. Draw the circuit diagram of DAC (digital to analog converter) using R-2R ladder network with 4 bit input and explain its working. **3**  
 iii. Draw the block diagram of dual slop A/D converter and explain its working. **5**
- OR iv. Explain the working principal of successive approximation A/D converter with block diagram. **5**

\*\*\*\*\*

**Marking Scheme**

Q.1	i.	$I_C = \beta I_B + \dots\dots\dots$ (c) $I_{CEO}$	<b>1</b>	Q.3	i.	Types of IC regulators – 0.5 mark each (0.5 mark * 4 = 2 marks)	<b>2</b>
	ii.	If the value of $\alpha$ is 0.9, then value of $\beta$ is $\dots\dots\dots$ (a) 9	<b>1</b>		ii.	Op-amp based current limiting circuit – 1 mark It's working. – 2 marks	<b>3</b>
	iii.	In an unregulated power supply, if input a.c. voltage increases, the output voltage $\dots\dots\dots$ (a) Increases	<b>1</b>		iii.	SMPS regulator circuit diagram – 2 marks Their working with various functional block diagram – 3 marks	<b>5</b>
	iv.	A Zener diode is used as a voltage regulating device (a) Shunt	<b>1</b>	OR	iv.	Transistor based voltage series and voltage shunt regulators circuit diagram - 2 marks Its working – 3 marks	<b>5</b>
	v.	One condition for oscillation is $\dots\dots\dots$ (a) A phase shift around the feedback loop of $180^\circ$	<b>1</b>	Q.4	i.	Barkhausen Criteria for oscillators each criteria have 1 mark (1 mark * 2 = 2 marks)	<b>2</b>
	vi.	In Colpitt's oscillator, feedback is obtained..... (c) From the centre of split capacitors	<b>1</b>		ii.	Circuit diagram of phase shift oscillator – 1 mark Its Working principal – 2 marks	<b>3</b>
	vii.	How is a J-K flip-flop made to toggle? (d) $J = 1, K = 1$	<b>1</b>		iii.	Circuit diagram of active high pass filter – 1 mark Working principal - 2 marks Gain expression for it – 2 marks	<b>5</b>
	viii.	How many flip-flops are required to make a MOD-32 binary counter? (d) 5	<b>1</b>	OR	iv.	Block diagram of 555 timer - 2 marks Its working principal – 3 marks	<b>5</b>
	ix.	A 4-bit R/2R digital-to-analog (DAC) converter has a reference of 5 volts. What is the analog output for the input code 0101? (b) 3.125 V (d) -3.125 V	<b>1</b>	Q.5	i.	Race around condition – 2 marks How to remove Race around condition – 1 mark	<b>3</b>
	x.	What is the major advantage of the R/2R ladder digital-to-analog (DAC), as compared to a binary-weighted digital-to-analog DAC converter? (a) It only uses two different resistor values.	<b>1</b>		ii.	4 bit ring counter circuit – 3 marks Its working – 4 marks	<b>7</b>
Q.2	i.	Diagram Ebers Moll model for PNP transistor – 2 marks Explanation Ebers Moll model for PNP transistor – 2 marks	<b>4</b>	OR	iv	Decade counter using D flip flop – 3 marks Calculation for counter and explanation – 4 marks	<b>7</b>
	ii.	Calculation of $I_B = 20 \text{ GA}$ – 3 marks Calculation of $V_{CE} = 5 \text{ v}$ - 3 marks	<b>6</b>	Q.6	i.	Any 3 difference between analog and digital systems	<b>2</b>
OR	iii.	Common emitter amplifier circuit h model – 2 marks Calculation input impedance, voltage gain - 4 marks	<b>6</b>		ii.	DAC (digital to analog converter) circuit ladder – 1 mark DAC circuit ladder working – 2 marks	<b>3</b>
					iii	Block diagram of dual slop A/D converter – 2 marks Dual slop A/D converter working – 3 marks	<b>5</b>
				OR	iv	Successive approximation A/D converter with block diagram – 2 marks Working principal of Successive approximation A/D converter – 3 marks	<b>5</b>

\*\*\*\*\*