

[4]

- Q.5 i. Define Zener diode and its application also draw its equivalent circuit. 2
ii. What is basic difference between BJT, MOSFET and JFET 3
iii. Define α and β of a transistor and derive the relationship between them. 5
OR iv. Explain full wave diode rectifier with Circuit diagram, input-output waveform and efficiency. 5
- Q.6 i. Convert these number as given. 2
(a) $(365.24)_8 = ()_{10}$ (b) $(68.4B)_{16} = ()_8$
ii. Define Flip-Flop also draw the block diagram and truth table of basic SR flip flop. 3
iii. Explain full adder with truth table, boolean expression and block diagram. 5
OR iv. Draw the basic gates (AND, OR & NOT) using universal NAND and NOR gate. 5

Total No. of Questions: 6

Total No. of Printed Pages: 4

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2017
EN3ES04 Basic Electrical and Electronics Engineering
Programme: B.Tech. Branch/Specialisation: All

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.


- Q.1 i. A network which does not have either voltage sources or current sources is called. 1
(a) Active network (b) Passive network
(c) Resistive network (d) Dummy network
- ii. What will be the current passing through the ring shaped air cored coil when number of turns is 800 and ampere-turn are 3200 1
(a) 0.25 (b) 2.5 (c) 4.0 (d) 0.4
- iii. The power factor at the time of resonance is 1
(a) Lagging (b) Leading (c) Unity (d) Zero
- iv. When the power transferred to the load is maximum, the efficiency of power transfer is. 1
(a) 25% (b) 75% (c) 50% (d) 100%
- v. In ideal transformer the no load current lags behind the applied voltage by an angle of 1
(a) 90 degree (b) 180 degree (c) 120 degree (d) 0 degree
- vi. Which losses are load dependent losses in transformer 1
(a) Core loss (b) Copper loss (c) Iron loss (d) All of these
- vii. When a pn junction is reverse biased 1
(a) The width of depletion layer increases
(b) It offers a high resistance
(c) A small current flows through it because of minority carriers
(d) All of these

P.T.O.


[2]

- viii. Which of the following is valid for both P-N-P as well as N-P-N transistors. 1
- The emitter injects holes into the base region
 - The electron are the minority carriers in base region
 - The EB is forward biased for active operation
 - When biased in active region, current flows into emitter terminal.
- ix. 1's complement subtraction of (11010 – 1101) will be 1
- 1101
 - 1011
 - 1100
 - None of these
- x. Addition of $(634)_8 + (152)_8$ will be 1
- 1006
 - 886
 - 582
 - None of these

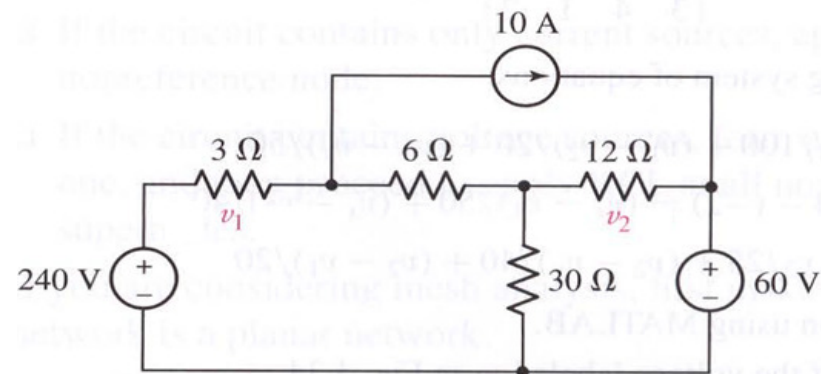- Q.2 i. Define the term Ideal and Practical voltage and current sources. 2
- ii. Compare the electrical and magnetic circuit with any four similarities and any two dissimilarity. 3
- iii. Find V_1 and V_2 using nodal analysis. 5




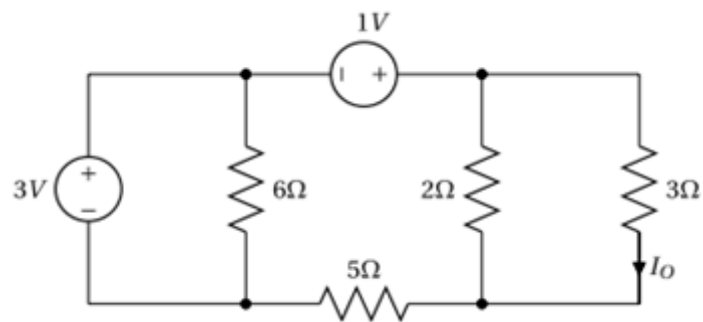- OR iv. Find I_o (current through 3 ohm resistance) using Mesh analysis. 5



[3]

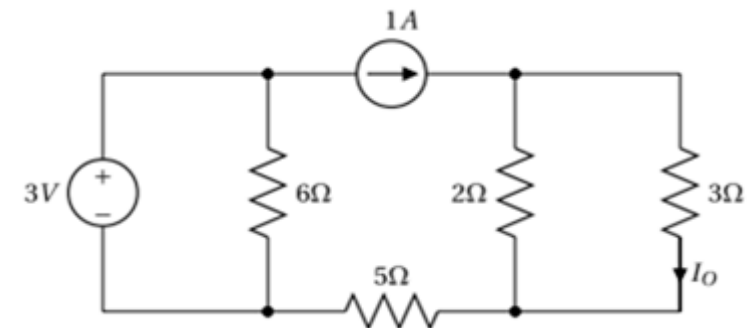- Q.3 i. Define the maximum power transfer theorem and formulate the maximum power transferred. 2
- ii. Find I_o (current through 3 ohm resistance) using thevenin or Norton theorem. 3



- iii. Two circuit , the impedance of which are given by $Z_1 = (10 + j15)$ ohm and $Z_2 = (6 - j8)$ ohm are connected in parallel. If the total current supplied is 15 Amp, what is power taken by each branch. Draw the phasor diagram also. 5

- OR iv A choke coil has a resistance of 2 ohm and a inductance of 5 H. A capacitor C is connected in series with a choke coil and the combination is fed from from 230 volt,50 Hz source. what should be the value of C so that the voltage across the capacitor is 250 volts. 5

- Q.4 i. Define the efficiency and voltage regulation of transformer with formula. 2
- ii. How three phase induction motor run and why it is called a asynchronous motor. 3
- iii. Obtain approximate equivalent circuit of a given 200/2000 V, 50 Hz single phase 30 KVA transformer having the following test result. 5

O.C. Test: 200 V, 6.2 A, 360 W on l.v. side

S.C. Test: 75 V, 18 A, 600 W on h.v. side


- OR iv Draw the phasor diagram of transformer with (a) No load condition (b) lagging power factor also write the proccedure for drawing the phasor. 5

P.T.O.

Marking Scheme

- Q.1 i. A network which does not have either voltage sources or current sources is called **1**
 (b) passive network
- ii. What will be the current passing through the ring shaped air cored coil when number of turns is 800 and ampere-turn are 3200 **1**
 (c) 4.0
- iii. The power factor at the time of resonance is **1**
 (c) Unity
- iv. When the power transferred to the load is maximum, the efficiency of power transfer is **1**
 (c) 50%
- v. In ideal transformer the no load current lags behind the applied voltage by an angle of **1**
 (a) 90 degree
- vi. Which losses are load dependent losses in transformer **1**
 (b) Copper loss
- vii. When a pn junction is reverse biased **1**
 (d) All of these
- viii. Which of the following is valid for both P-N-P as well as N-P-N transistors. **1**
 (c) The EB is forward biased for active operation
- ix. 1's complement subtraction of (11010 – 1101) will be **1**
 (a) 1101
- x. Addition of $(634)_8 + (152)_8$ will be **1**
 (a) 1006

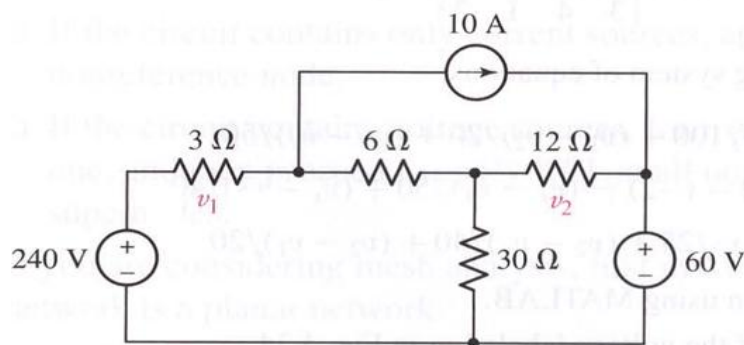- Q.2 i. 1 marks for each definition (1 * 2 = 2 marks) **2**
- ii. 2 marks for any 4 similarities **3**
 1 marks for any 2 disimilarities
- iii. **5**




2 marks for nodal equation
 $3V_a - V_b = 420$(1) node a
 $-10V_a + 17V_b = 300$(2) node b

2 marks for nodal voltage
 $V_a = 7440/41 = 181.46$ volt
 $V_b = 5100/41 = 124.39$ volt

1 marks for desired voltage (v_1 & v_2)
 $V_1 = 58.54$ volt and $V_2 = 64.39$

OR iv.

5

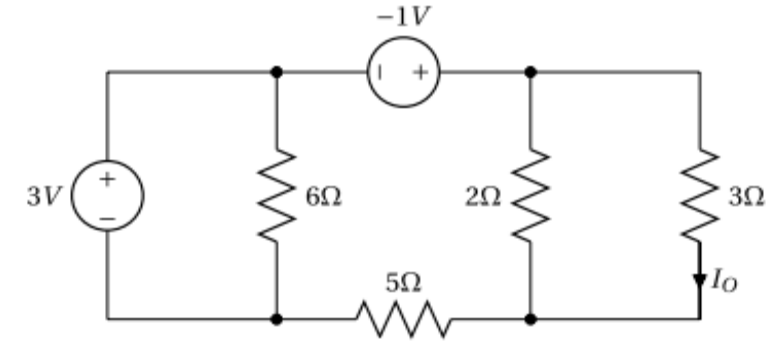

2 marks for loop equation
 $-6I_1 + 6I_2 = -3$ (1) loop 1
 $-6I_1 + 13I_2 - 2I_3 = 1$(2) loop 2
 $2I_2 - 5I_3 = 0$(3) loop 3

2 marks for loop current
 $I_1 = 71/62 = 0.822$, $I_2 = 20/31 = 0.645$, $I_3 = 8/31 = 0.258$


1 marks for desired current (I_0)
 $I_0 = 0.258$ amp

- Q.3 i. 1 marks for definition **2**
 1 marks for formula

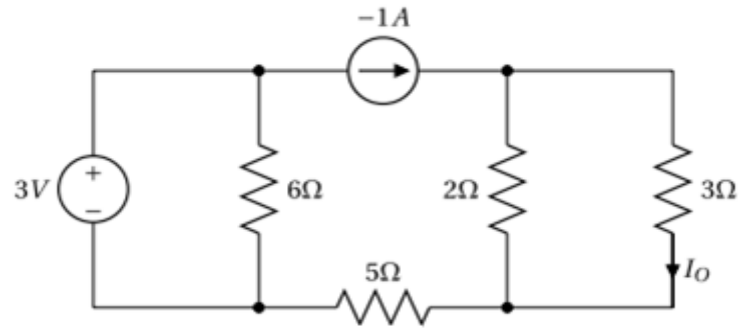- ii. 1 marks for thevenin voltage **3**
 $V_{th} = 1 * 2 = 2$ volt

1 marks for thevenin resistance
 $R_{th} = 2$ ohm

1 marks for load current
 $I_L = I_0 = 2/(2+3) = -2/5 = 0.4$ amp



- iii. **Solution:** $Z_1 = 10 + j15 = 18 \angle 56.3^\circ$ 5
 $Z_2 = 6 - j8 = 10 \angle -53.13^\circ$
 $Z_1 + Z_2 = 16 + j7 = 17.46 \angle 23.63^\circ$
 Branch Current, $I_1 = I * Z_1 / (Z_1 + Z_2)$
 $= 8.89 \angle -76.76^\circ$
 Branch Current, $I_2 = I * Z_2 / (Z_1 + Z_2)$
 $= 15.46 \angle 32.6^\circ$
2 marks for I_1 & I_2 in each branch

Power taken by first branch $P_1 = I^2 R = 737.88$ watt
 Power taken by second branch $P_2 = I^2 R = 1434$ watt

2 marks for P_1 & P_2 in each branch

- OR iv **1 mark** for phasor diagram 5
Solution:
 $R = 2 \text{ ohm}$, $L = 5 \text{ H}$, $X_L = 2\pi f L = 1570 \text{ ohm}$
 $V_c = I X_c = 250$, and $I = V/Z$
 $X_c = 817.7$
 $C = 3.89 \text{ microfarad}$
 1 marks for inductive reactance
 2 marks for current equation
 2 marks for capacitance value

- Q.4 i. 1 marks for each definition 2
 ii. 1.5 marks for each part ($1.5 * 2 = 3$ marks) 3
 iii. **Solution:** 5
2 marks for core parameter
 OC Test:
 $I_w = 1.8 \text{ A}$, $I_m = 5.93 \text{ A}$, $R_e = 111.11 \text{ ohm}$, $X_m = 33.7 \text{ ohm}$
2 marks for winding parameter
 SC Test:
 $R_{eq} = 1.85 \text{ ohm}$, $Z_{eq} = 4.167 \text{ ohm}$,
 Referred to lv side $Z_{01} = 0.04167 \text{ ohm}$, $R_{01} = 0.0185 \text{ ohm}$, $X_{01} = 0.0373 \text{ ohm}$

- OR iv **1 marks** for equivalent circuit diagram 5
 2 marks for part a
 2 marks for part b
 1 marks for procedure.
- Q.5 i. 1 marks for definition and application 2
 1 marks for equivalent
- ii. 1 marks for each basic difference between them. ($1 * 3 = 3$ marks) 3
- iii. 2 marks for definition 5
 3 marks for derivation for relationship
- OR iv 2 marks for circuit diagram 5
 1 marks for waveform
 2 marks for efficiency derivation
- Q.6 i. Convert these number as given. 2
 (a) $(365.24)_8 = (245.3125)_{10}$
 (b) $(68.4B)_{16} = (150.226)_8$
 1 marks for each part ($1 * 2 = 2$ marks)
- ii. 1 marks for definition 3
 1 marks for block diagram
 1 marks for truth table
- iii. 1 marks for truth table 5
 2 marks for boolean expression
 2 marks for block diagram
- OR iv. 2.5 marks for NAND gate 5
 2.5 marks for NOR gate
