

- Q.5 i. Obtain the transform current $I(s)$ in the circuit shown in Fig.11 below assuming initial conditions to be zero. **4**
 ii. The switch K is at 1 for long time and is moved from 1 to 2 at $t = 0$. Determine i_L for $t > 0$ in Fig.12. **6**

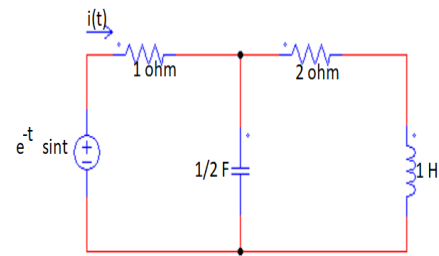


Fig. 11

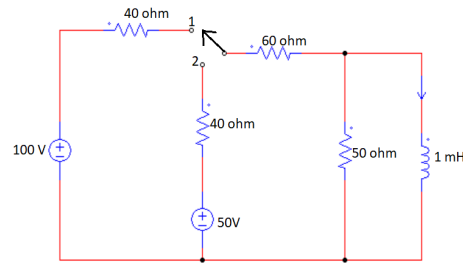


Fig. 12

- OR iii. In the network shown in Fig.13 below the initial voltage on C_1 is 2 volt and on C_2 is 1 Volt. At $t=0$, the switch is closed. Determine $i(t)$, $v_1(t)$ and $v_2(t)$ for $t > 0$ using Laplace Transformation. **6**

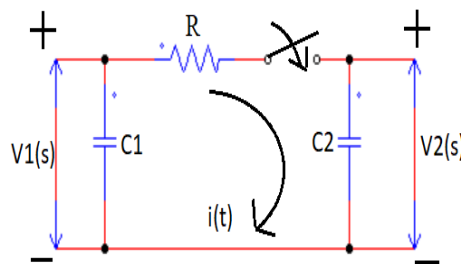


Fig.13

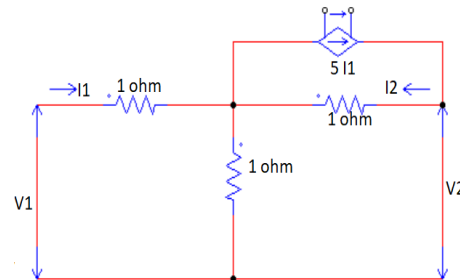


Fig.14

- Q.6 Attempt any two:
 i. Calculate h-parameters for the circuit shown above in Fig.14. **5**
 ii. Find the first Cauer form of R-C network for impedance function **5**

$$Z(s) = \frac{(s^2 + 7s + 10)}{s^2 + 4s + 3}$$

 iii. Find ABCD parameters in terms of Z and Y parameter? **5**

Enrollment No.....



Faculty of Engineering
 End Sem (Odd) Examination Dec-2018
 EE3CO07/EX3CO07 Circuit Analysis and Synthesis
 Programme: B.Tech. Branch/Specialisation: EE/EX

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. The total power in a series circuit is 10 watt there are five equal value resistors in the circuit. How much power does each resistor dissipate **1**
 (a) 10W (b) 5W (c) 2W (d) 1W
 ii. When the superposition theorem is applied to any circuit, the dependent voltage source in that circuit is always **1**
 (a) Active (b) Opened (c) Shorted (d) None of these
 iii. The tie-set schedule gives the relation between **1**
 (a) Branch current and link currents
 (b) Branch voltage and link voltage
 (c) Branch current and link voltage
 (d) None of the above
 iv. The reciprocity theorem is applicable to **1**
 (a) Linear network only (b) Bilateral networks only
 (c) Linear bilateral networks (d) Neither of the two
 v. For a two port network to be reciprocal **1**
 (a) $Z_{11}=Z_{22}$ (b) $Y_{21}=Y_{12}$ (c) $h_{21}=-h_{12}$ (d) $AD-BC=0$
 vi. For a two port bilateral network, the three transmission parameter are given by $A=6/5$; $B=17/5$; and $C=1/5$. What is the value of D? **1**
 (a) 1 (b) 1/5 (c) 7/5 (d) 5
 vii. The transient response occurs **1**
 (a) Only in resistive circuits (b) Only in Inductive circuits
 (c) Only in capacitive circuits (d) Both (b) & (c)
 viii. The transient current in a loss-free LC circuit when excited from an ac source is an _____ sine wave **1**
 (a) Undamped (b) Overdamped
 (c) Underdamped (d) Critically damped

[2]

- ix. In the first Foster form, the presence of last element inductor L_∞ indicates. **1**
 (a) Pole at $\omega=0$ (b) Pole at $\omega=\infty$
 (c) Zero at $\omega=0$ (d) Zero at $\omega=\infty$
- x. The final value theorem is used to find the **1**
 (a) Steady state value of the system output
 (b) Initial value of the system output
 (c) Transient behaviour of the system output
 (d) None of these

- Q.2 i. Write the tie set matrix and determine the KVL equation and also **2**
 calculate the loop currents for the network shown in Fig.1 below.
- ii. Draw the graph for the network shown in Fig.2 below and determine the **3**
 number of possible trees.

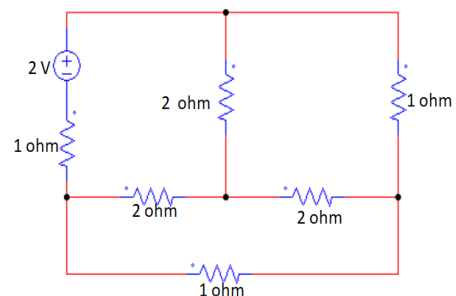


Fig.1

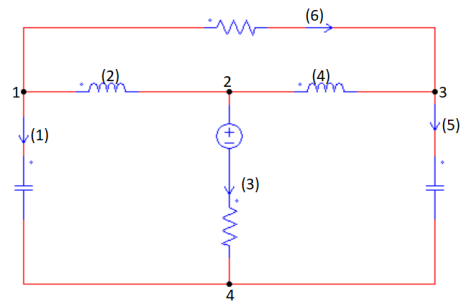


Fig.2

- iii. Find the current passing through 6Ω resistors in Fig.3. **5**
- OR iv. Find the power loss in 2Ω resistor by Maxwell loop method in Fig.4. **5**

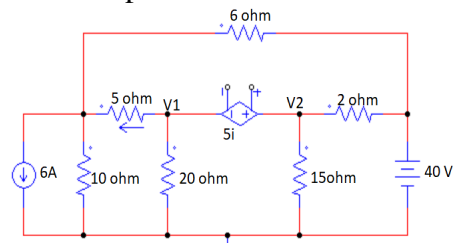


Fig.3

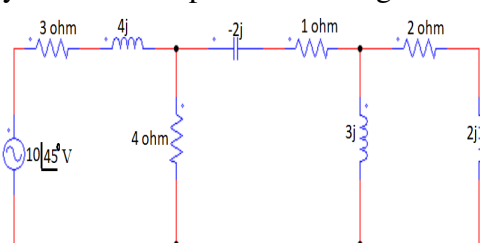


Fig.4

- Q.3 i. State and prove Norton's theorem? **2**
- ii. If we change the load $5+2j$ connected across terminals AB by $1+j\Omega$ then **3**
 find the change in current drawn from the supply by compensation theorem in Fig.5?

[3]

- iii. Find the thevenin's equivalent circuit and then find the power loss in 5Ω **5**
 resistor for the circuit shown in Fig.6 below

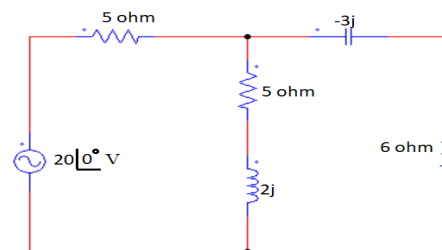


Fig. 5

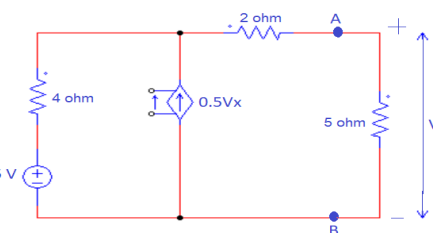


Fig. 6

- OR iv. Find the voltage drop across the capacitor by superposition theorem in **5**
 Fig.7?

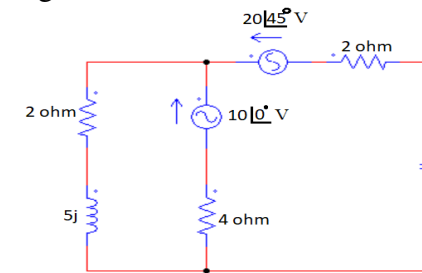


Fig.7

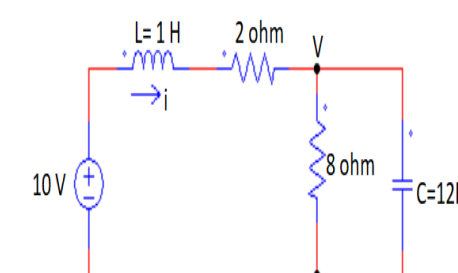


Fig.8

- Q.4 i. In the circuit find $i(\infty)$ and $v(\infty)$ i.e., the steady state values of the network **2**
 shown in Fig.8 above.
- ii. In the network Fig.9 below switch K is closed at $t=0$. Determine **8**
 $i_C, i_L, \frac{dv_C}{dt}, \frac{dv_L}{dt}$ at $t=0^+$.
- OR iii. Find the expression for current $i(t)$ for $t > 0$ if switch is closed at $t=0$ in **8**
 Fig.10.

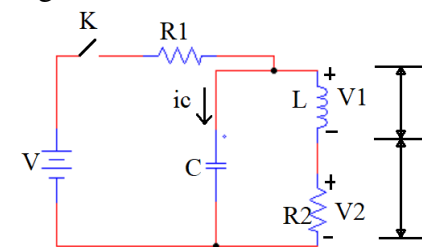


Fig.9

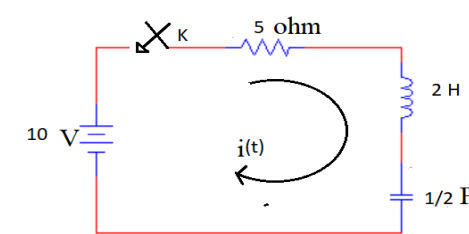


Fig.10


Marking Scheme

EE3CO07/EX3CO07 Circuit Analysis and Synthesis

Q.1	i.	The total power in a series circuit is 10 watt there are five equal value resistors in the circuit. How much power does each resistor dissipate (c) 2W	1	1
	ii.	When the superposition theorem is applied to any circuit, the dependent voltage source in that circuit is always (a) active	1	1
	iii.	The tie-set schedule gives the relation between (a) Branch current and link currents	1	1
	iv.	The reciprocity theorem is applicable to (c) Linear & bilateral networks	1	1
	v.	For a two port network to be reciprocal (c) $h_{21} = -h_{12}$	1	1
	vi.	For a two port bilateral network, the three transmission parameter are given by $A=6/5$; $B=17/5$; and $C=1/5$. What is the value of D? (c) $7/5$	1	1
	vii.	The transient response occurs (d) Both (b) & (c)	1	1
	viii.	The transient current in a loss-free LC circuit when excited from an ac source is an----- sine wave (a) Undamped	1	1
	ix.	In the first Foster form, the presence of Last element Inductor L_{∞} indicates. (b) pole at $\omega=\infty$	1	1
	x.	The final value theorem is used to find the (a) Steady state value of the system output	1	1
Q.2	i.	Tie Set Matrix & KVL Equation Loop Currents	2 marks 1 mark	3
	ii.	Draw the graph Determine the number of possible trees.	1 mark 2 marks	3
	iii.	For Equations Current Passing through 6 ohm resistor= 5 Amp	3 marks 1 mark	4
OR	iv.	For Equations power lost in 2Ω resistor= 0.9934	3 marks 1 mark	4

Q.3	i.	Statement Proof	1 mark 1 mark	2
	ii.	Change in Current, $I = 1.444\angle 21.52^\circ$ Compensation Voltage, $V_c = 2.043\angle 230.47^\circ$	1.5 marks 1.5 marks	3
OR	iii.	Thevenins Equivalent ($V_{th} = 5V$, $I_{sc} = 0.55$ Amp, $R_{th} = 9\ \Omega$) Power Loss in 5 ohm resistor= 637mW	3 marks 2 marks	5
OR	iv.	Current Passing through the capacitor, $I_C = 1.4092.674j$ Amp Voltage across capacitor, $V_c = 5.348 + 2.818j$ Volt	2.5 marks 2.5 marks	5
Q.4	i.	$i(\infty) = 1$ Amp $v(\infty) = 8$ Volt	1 mark 1 mark	2
	ii.	$I_C(0+) = V/R_1$ $I_L(0+) = 0$ $dv_C/dt(0+) = I_C/C$ $dv^2/dt^2(0+) = 0$	2 marks 2 marks 2 marks 2 marks	8
OR	iii.	At $t > 0$ $i(t) = k_1 e^{-0.5t} + k_2 e^{-2t}$ At $t = 0$, $i(t) = 3.33 e^{-0.5t} - 3.33 e^{-2t}$	4 marks 4 marks	8
Q.5	i.	$Z(s) = \frac{(s^2 + 4s + 6)}{s^2 + 2s + 2}$ $I(s) = \frac{1}{s^2 + 4s + 6}$	2 marks 2 marks	4
	ii.	$i(t) = 0.5 - 0.5 e^{-\left(\frac{105}{3}\right)t} + e^{-\left(\frac{105}{3}\right)t}$	6 marks	6
OR	iii.	$i(t) = \frac{1}{R} e^{-\left(\frac{C_1 + C_2}{C_1 C_2 R}\right)t}$ $v_1(t) = 2 \frac{C}{C_1} [1 - e^{-\frac{t}{RC}}]$ $V_2(t) = 1 \frac{C_1}{C_1 + C_2} e^{-\left(\frac{C_1}{C_1 + C_2}\right)t} + \frac{C_1}{(C_1 + C_2)}$	2 marks 2 marks 2 marks	6
Q.6	Attempt any two:			
	i.	ABCD Parameters in terms of Z ABCD Parameters in terms of Y	2.5 marks 2.5 marks	5

ii.

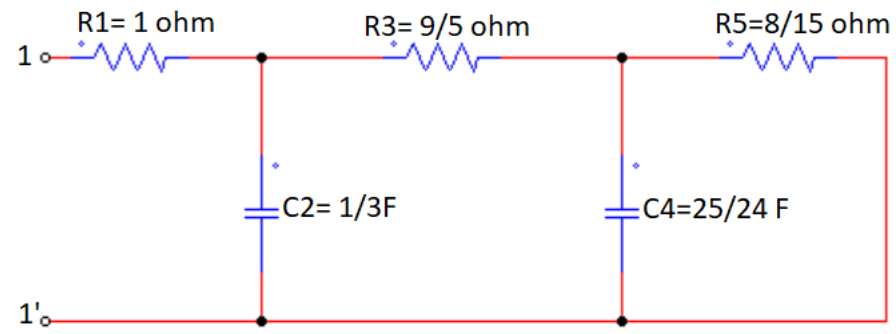

5

- iii. $h_{11} = 1\Omega$
 $h_{12} = 1/2$
 $h_{21} = 3$
 $h_{22} = 1/2 \text{ mho}$

1.25 marks
1.25 marks
1.25 marks
1.25 marks

5
