

[4]

- OR iii. Write need of starters. Explain working of capacitor start single phase induction motor. **8**
- Q.6 i. Draw the circuit symbol of Zener diode, UJT, MOSFET and SCR. **2**
- ii. Compare half wave and full wave rectifier with the help of their circuit and input, output voltage waveforms. **8**
- OR iii. Define gain. Explain working of transistor as an amplifier. **8**

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2017
ME2ES07 Basics of Electrical and Electronics
Engineering

Programme: Diploma

Branch/Specialisation: ME

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. If 125V is applied across a 250V, 100W bulb. The power consumption will be **1**
- (a) 100W (b) 50W
(c) 25W (d) 12.5W
- ii. The practical unit of electrical energy is, **1**
- (a) Joule-second (b) Watts-second
(c) Kilowatt-hour (d) Watt-hour
- iii. The power factor of a purely inductive circuit is, **1**
- (a) Lagging (b) Leading
(c) Zero lagging (d) Unity
- iv. In a balanced 3-phase delta connected system, the relationship between the rms values of line currents and the phase current is given by, **1**
- (a) $I_L = I_{ph}$ (b) $I_L = \sqrt{3} I_{ph}$
(c) $I_{ph} = \sqrt{3} I_L$ (d) $I_L = \sqrt{2} I_{ph}$
- v. The rotating part of the dc machine is generally called, **1**
- (a) Stator (b) Rotor
(c) Pole (d) Armature
- vi. The commutator of a dc motor serves the purpose of, **1**
- (a) Changing ac into dc (b) Converting dc into ac
(c) Reducing friction (d) Avoiding arc at the brushes

P.T.O.

[2]

- vii. Transformers basically work on, 1
 (a) Mutual induction (b) Self induction
 (c) Static induction (d) None of these
- viii. 3-phase slip-ring induction motor, when fed from a 3-phase, f Hz supply, 1
 operates at a slip, s . Then the frequency of induced emf in the stator and rotor are, respectively given by,
 (a) sf, f (b) f, f
 (c) sf, sf (d) f, sf
- ix. Transistor can be used as an amplifier when it is operated 1
 (a) In the saturation region
 (b) In the cut-off region
 (c) In the active region
 (d) In both saturation & cut-off regions
- x. Ripple factor for a half-wave and full-wave rectifier circuit, respectively are 1
 (a) 0.48 and 1.21 (b) 0.48 and 0.121
 (c) 4.8 and 1.21 (d) 8.21 and 0.48

- Q.2 i. Enlist the name of sources available for DC and AC supply. Also write the standard voltages used in generation, transmission and distribution. 2
- ii. What is the statement of Ohm's law? Calculate the current flowing through the various resistances in the circuit shown in figure (1). 8

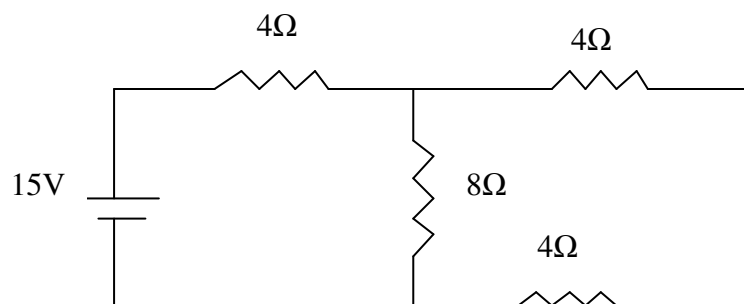


Figure (1)

- OR iii. Write the statement of Kirchhoff's voltage and current law. With the Kirchhoff's laws, solve the network shown in figure (2) and find the current in each branch. 8

[3]

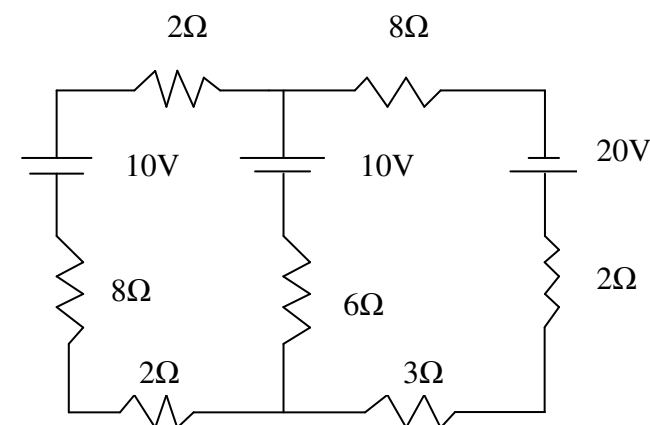


Figure (2)

- Q.3 i. Define frequency, average value, RMS value and form factor for the sinusoidal voltage wave. 2
- ii. Enlist power factor improving methods. A coil of resistance 20 ohms and inductance 0.5H is connected in series with a condenser of capacitance 100 micro-farad across a 230V, 50Hz supply. Determine – impedance, current of the circuit, power factor, voltage across the coil, and voltage across the condenser. 8
- OR iii. Compare star connection and delta connection of the three phase ac supply system. Also write advantages of three phase supply. 8
- Q.4 i. Write Fleming's left hand and right hand rule. 2
- ii. Enlist the main parts of a dc machine. Explain functions of each part. 8
- OR iii. Compare characteristics of DC series and shunt motor. Enlist electric shock preventive methods. 8
- Q.5 i. A 50kVA transformer has a voltage ratio of 3300/400V. Calculate the primary and secondary currents. 2
- ii. Describe the principle of operation of three phase induction motor. Also enlist applications of three phase induction motors. 8

ME2ES07 Basics of Electrical and Electronics Engineering

Marking Scheme

Q.1 i.	If 125V is applied across a 250V, 100W bulb. The power consumption will be (c) 25W	1	Q.3 i.	0.5 marks for each definition 0.5 mark * 4 = 2 marks	2
ii.	The practical unit of electrical energy is, (c) Kilowatt-hour	1	ii.	2 marks for power factor improving methods 6 marks for numerical 1 mark for current diagram 1 mark for finding each unknown quantities (1 mark * 5= 5 marks)	8
iii.	The power factor of a purely inductive circuit is, (c) Zero lagging	1	OR iii.	5 marks for comparison of star and delta connection 3 marks for advantages of three phase supply	8
iv.	In a balanced 3-phase delta connected system, the relationship between the rms values of line currents and the phase current is given by, (b) $I_L = \sqrt{3} I_{ph}$	1	Q.4 i.	1 mark for Fleming's left hand rule 1 mark for Fleming's right hand rule.	2
v.	The rotating part of the dc machine is generally called, (d) Armature	1	ii.	Parts of a dc machine 2 marks for diagram 6 marks for parts + explanation	8
vi.	The commutator of a dc motor serves the purpose of, (b) Converting dc into ac	1	OR iii.	5 marks for DC series and shunt motor 3 marks for electric shock preventive methods	8
vii.	Transformers basically work on, (a) Mutual induction	1	Q.5 i.	1 mark for primary currents 1 mark for secondary currents.	2
viii.	3-phase slip-ring induction motor, when fed from a 3-phase, f Hz supply, operates at a slip, s . Then the frequency of induced emf in the stator and rotor are, respectively given by, (d) f, sf	1	ii.	5 marks for principle of operation 3 marks for applications	8
ix.	Transistor can be used as an amplifier when it is operated (c) In the active region	1	OR iii.	3 marks for need of starters 5 marks for working of capacitor start	8
x.		1	Q.6 i.	0.5 for each circuit symbol 0.5 mark * 4 = 2 marks	2
Q.2 i.	1 mark for sources available for DC and AC supply 1 mark for standard voltages	2	ii.	4 marks for half wave rectifier 4 marks for full wave rectifier	8
ii.	2 marks for statement of Ohm's law 6 marks for Numerical 1 mark +1 mark = 2 marks for equation 1 mark +1 mark +1 mark +1 mark = 4 marks for current	8	OR iii.	2 marks for definition of gain 6 marks for working of transistor	8
OR iii.	3 marks for Kirchoff's voltage and current law. 5 marks for Numerical (2 marks for equation + 3 marks for current)	8			